

Fast Harmonic compensation in hybrid HVDC offshore system



Shangen Tian

David Camops-Gaona

Rafeal Pena-Alzola

Olimpo Anaya-Lara

20 Jan 2022

DeepWind 2022



□ Outline

- Motivation
- HVDC Technology
- Hybrid HVDC system
- Harmonics compensation controller
- Conclusion and future work

☐ Motivation




COP26 held in Glasgow in 2021

Many countries have proposed plans to reduce carbon emission


UK Government proposed a Zero Carbon 2050 Plan

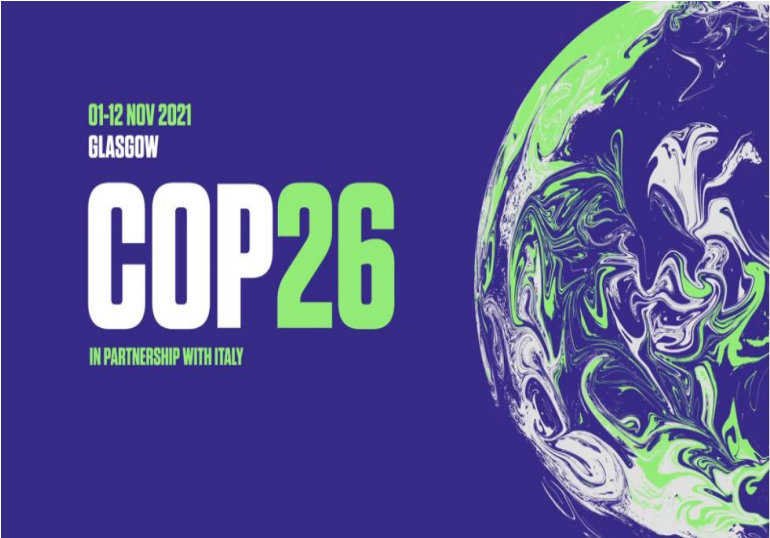Renewable energy plays an important role in power generation




HVDC Technology

LCC-HVDC

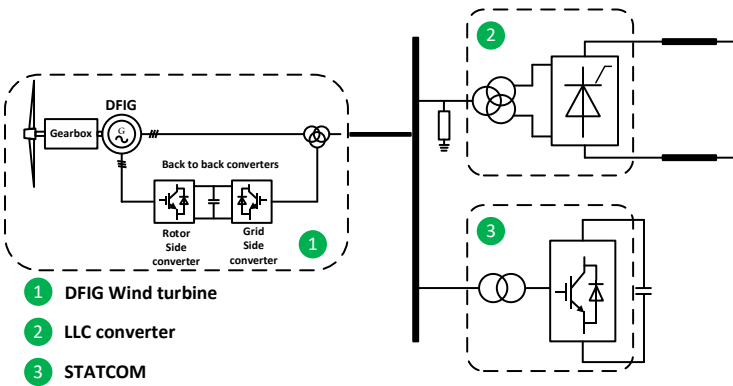


- ✓ Large capacity
- ✓ High reliability
- ✓ Low power losses
- ✗ External voltage source for commutation
- ✗ Larger filters

VSCC-HVDC

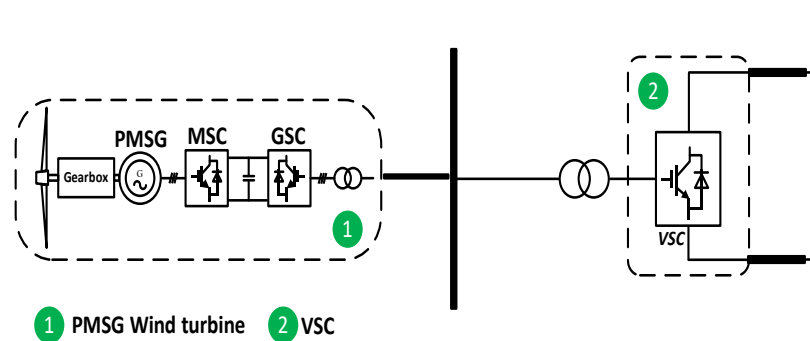


- ✓ Ability to control ac voltage as Grid forming converter
- ✓ Fault current limit ability
- ✗ High switching losses
- ✗ Filter required

DR-HVDC

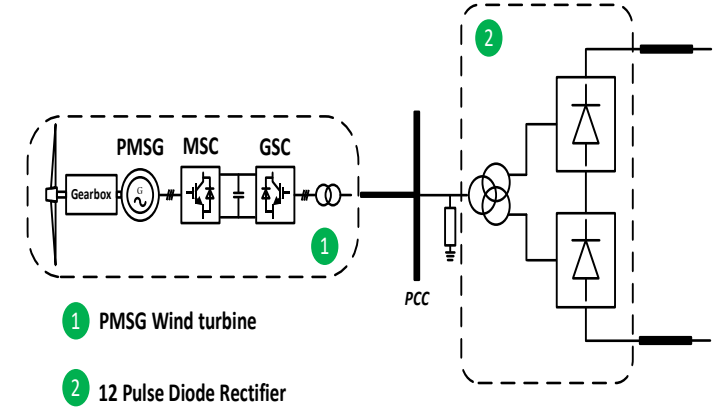

- ✓ Low cost
- ✓ High reliability
- ✓ Low power losses
- ✗ Uncontrollable
- ✗ Larger Filter required
- ✗ Need WTs converter as Grid forming converter

Hybrid HVDC system

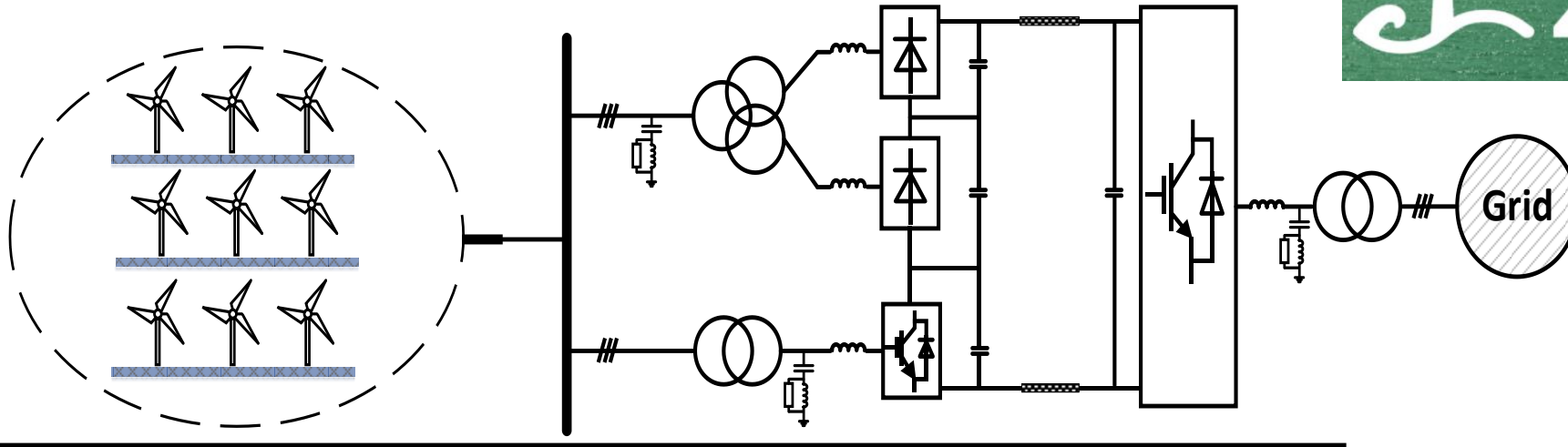

Hybrid converter components:

12 pulse diode rectifier (12P-DR) : uncontrollable power electronics device

2 level VSC/MMC: DC voltage controller and ac voltage controller

VSC functions as active power filter to cancel the harmonics current produced by 12P-DR

Advantages:

increase power capacity

low cost and small footprint


change power exchange between AC and DC side by control VSC DC voltage

Disadvantages:

no current loop control





complex transformer connection

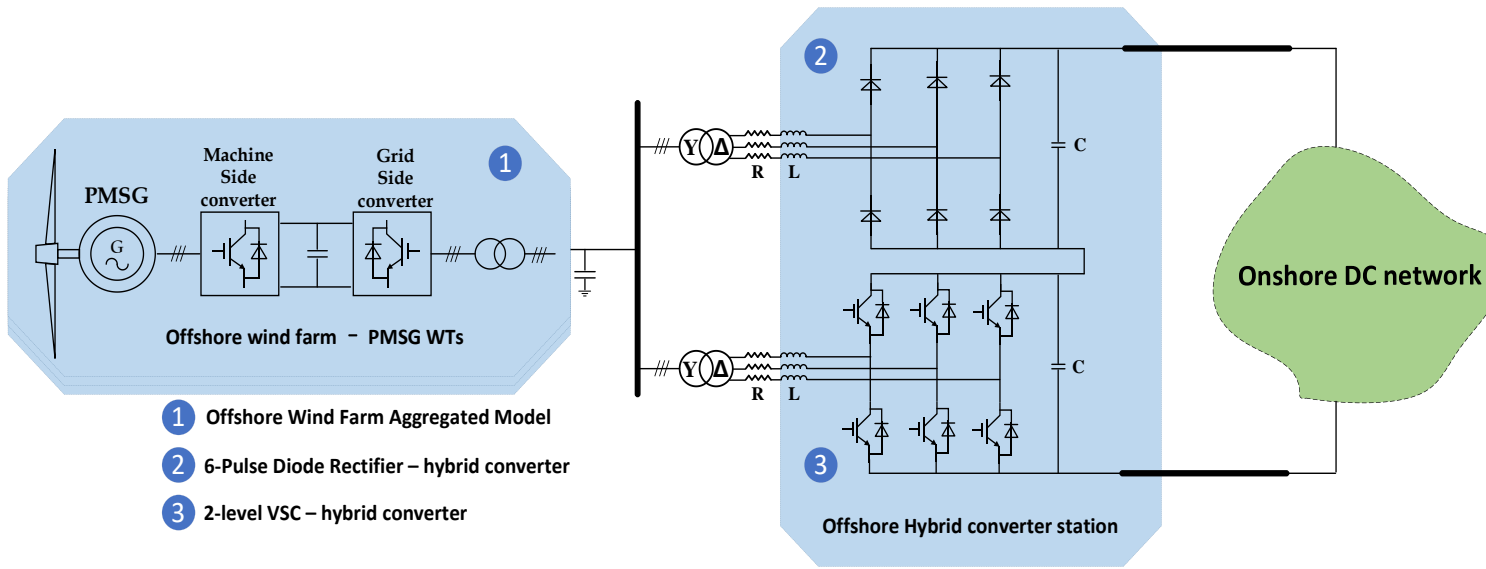
footprint and maintenance not discuss in detail








Offshore hybrid converter station:
2 Level VSC converter and 6P-DR in series connection

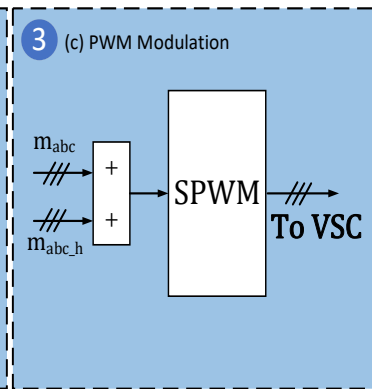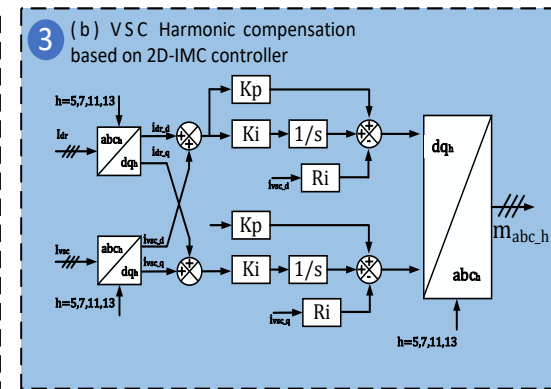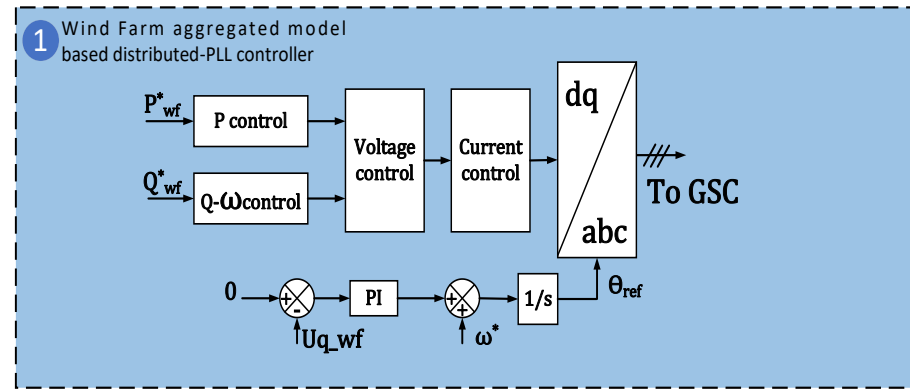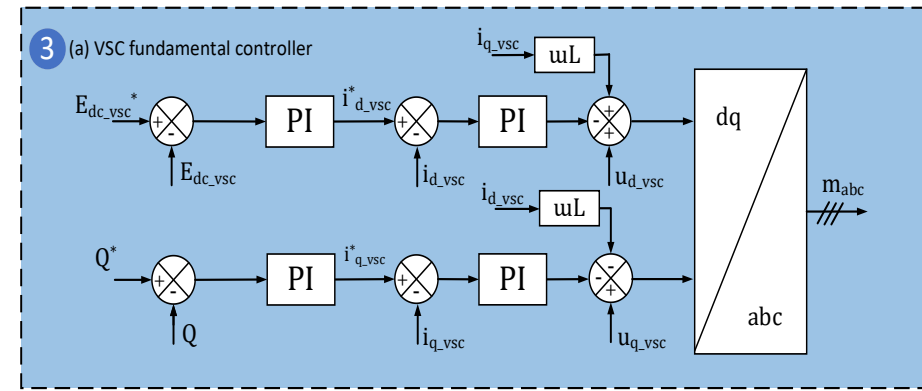- Simply transformer structure
- Improved control system
- Harmonics compensation using Serval Reference Frame(SRF) technique



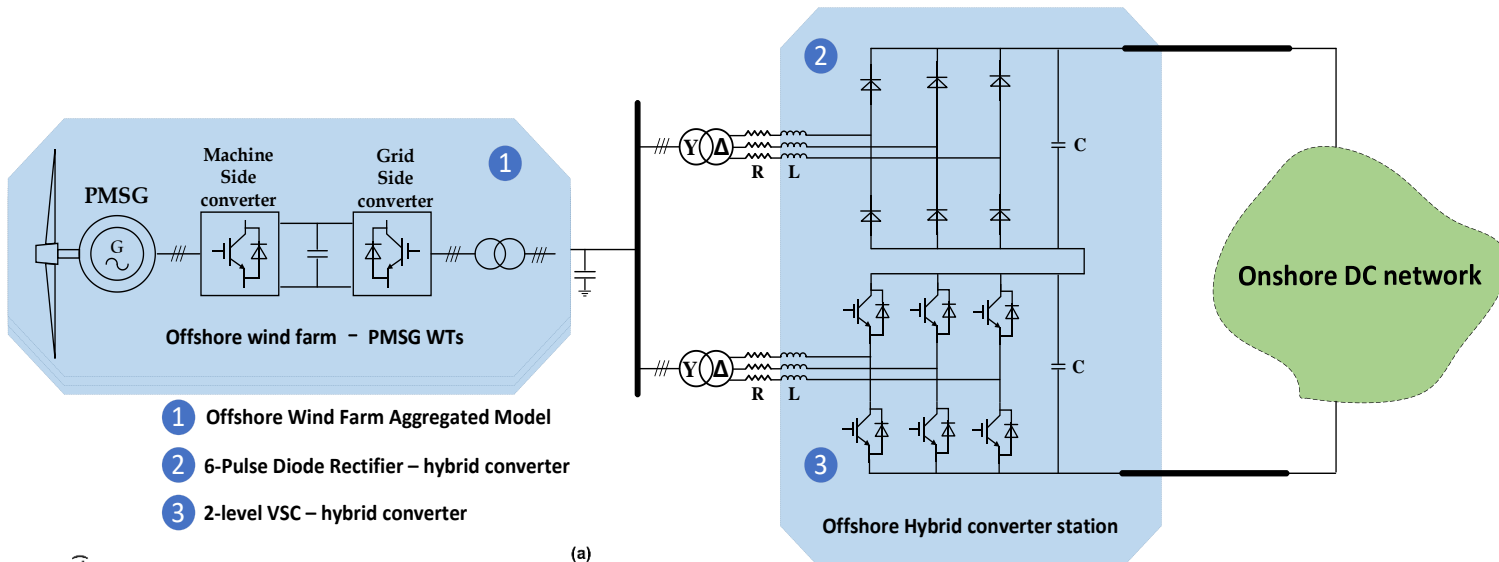

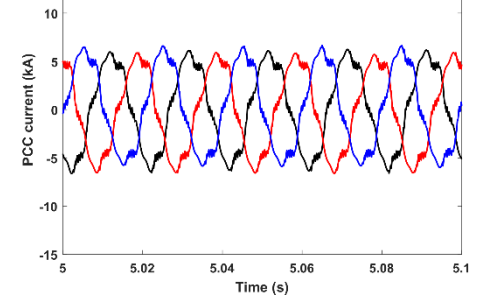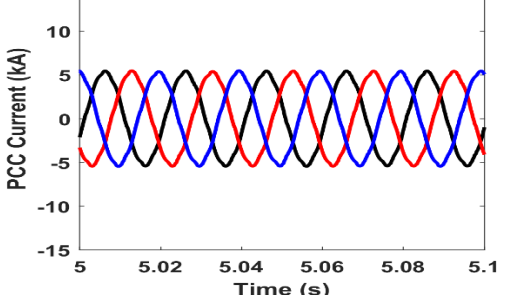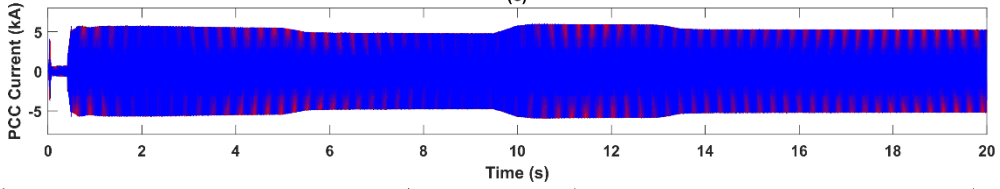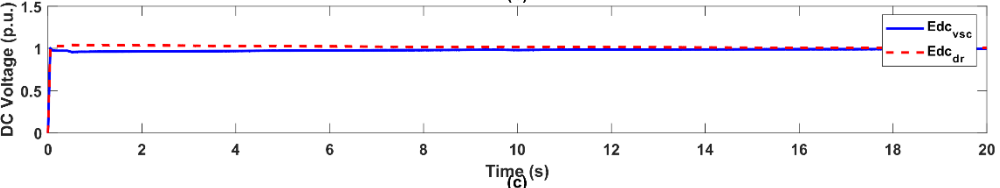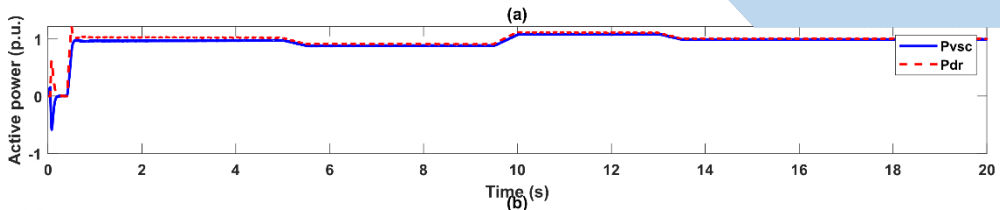- 1 Offshore Wind Farm Aggregated Model
- 2 6-Pulse Diode Rectifier – hybrid converter
- 3 2-level VSC – hybrid converter




- The simulation runs at different wind farm power levels to test the hybrid HVDC performance
- Figure (a) and (b) shows the active power and dc voltage of hybrid converter components. Transmitted power is proportional to its dc voltage
- For comparison
 - The PCC current with harmonics compensation controller (Right figure)
 - The PCC current without harmonics compensation controller (left figure)

Harmonics compensation using different controller




Proportional Resonant(PR)controller

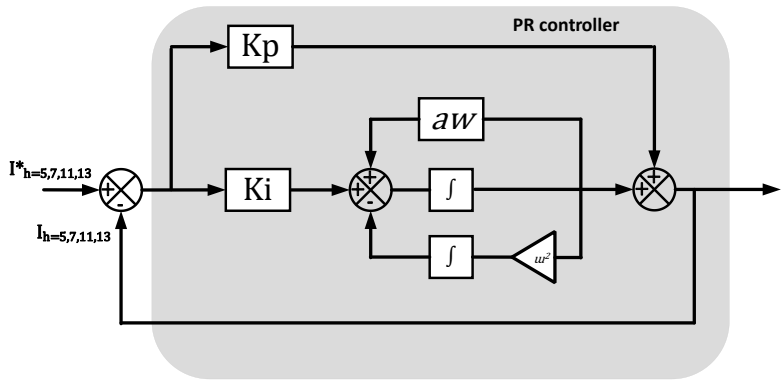


- By introducing an infinite gain at the desired resonant frequency
- ✓ Fast response for set-point changes
- ✗ Complex tuning process
- ✗ Easy influenced by Grid frequency variations resonant frequency will be tuned to reference frequency, infinite band is narrow

PI controller

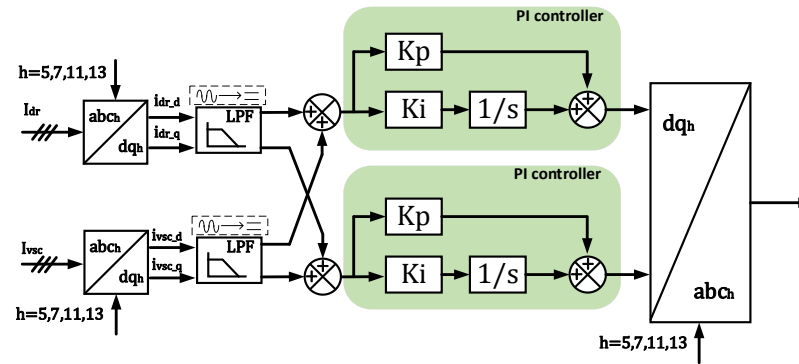

- Applied several synchronous dq harmonic frame to detect the harmonic current, then filter by low pass filter to get dc signal, finally tuning by PI controller
- ✓ Individual harmonics current controlled by dc signal
- ✓ Easy to tune
- ✗ Slow response to set point – the delay of Low pass filter in SRF technique.


2DF-IMC controller

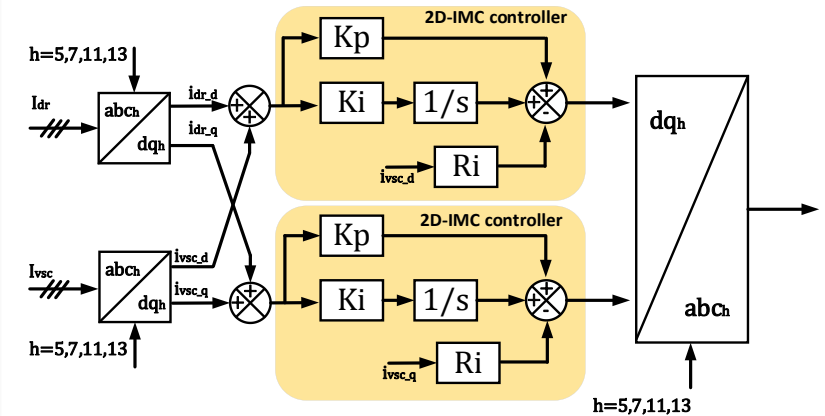


- Using two degrees of freedom internal model controller in SRF technique
- Remove the low pass filter to provide fast response to set point
- Harmonics component controlled by ac signals

❑ Harmonics compensation using different controller

- IMC controller

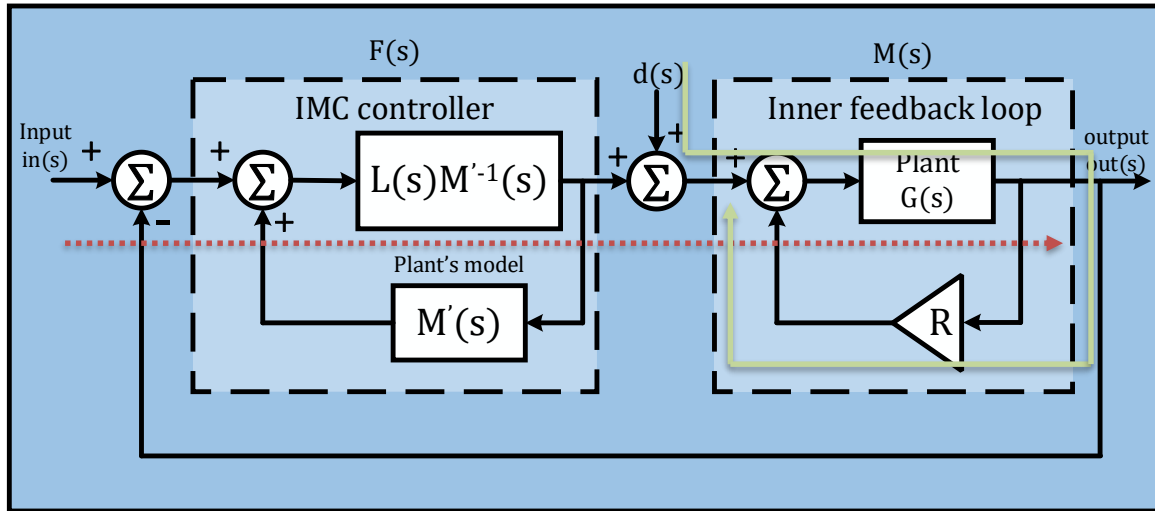

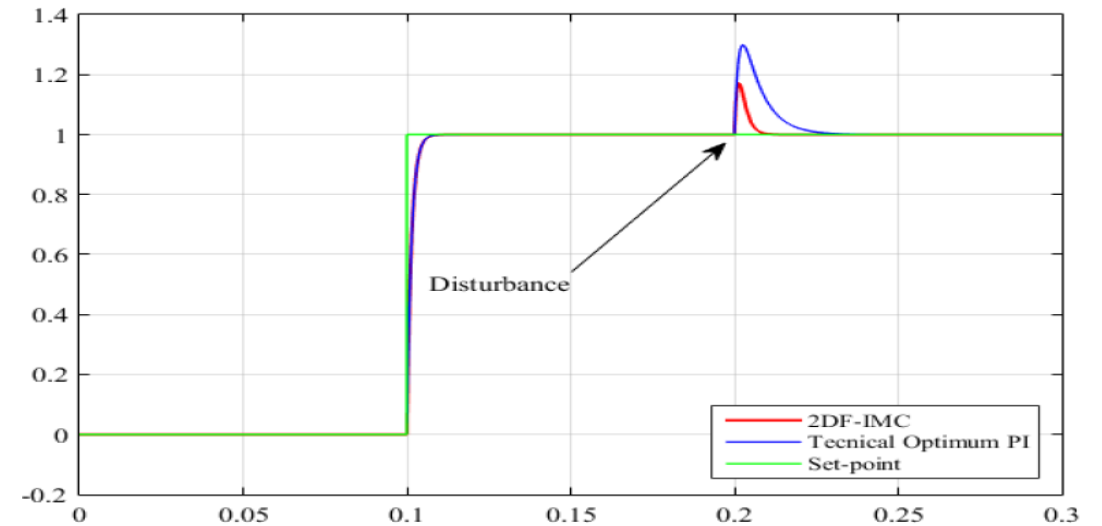- The Internal Model Controller (IMC) technique relies on the internal model principle
- The philosophy: control action over a plant can be achieved only if the control system includes, either implicitly or explicitly, some representation of the process to be controlled




In harmonics compensation control loop

Which components are the disturbance?





- Harmonics compensation controller using 2DF-IMC

➤ 2DF-IMC controller

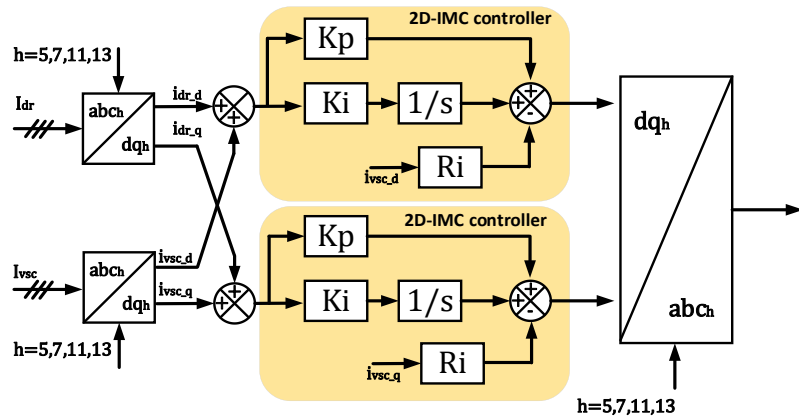

➤ PI controller

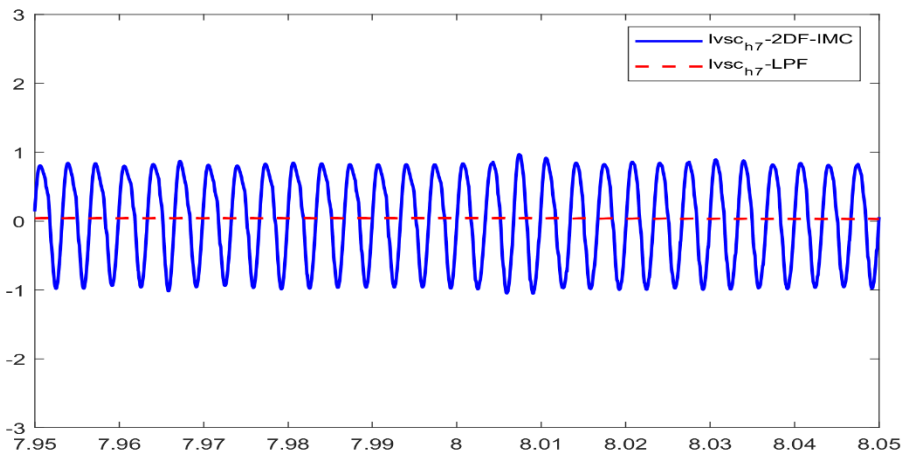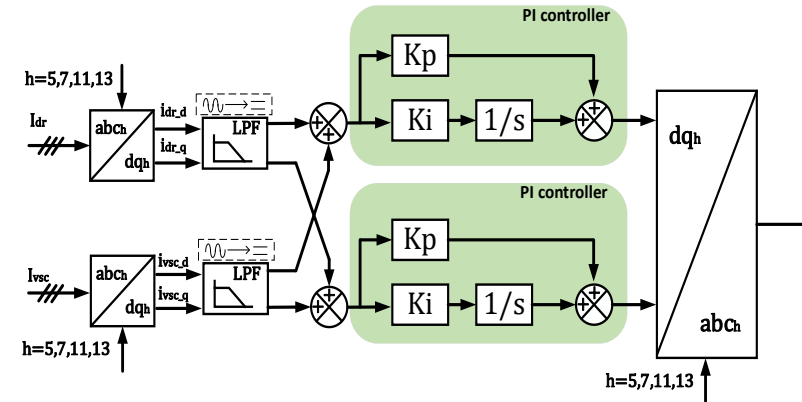

The sequence of the n harmonics and the sequence of the rest of harmonics:


$$i_{n_d} = \Gamma_n i_n \cos(\beta_n) + \sum_{k=1, k \neq n}^{\infty} \Gamma_k i_k \cos(-\Gamma_k [\Gamma_n n - \Gamma_k k](\omega_s t) + \beta_k)$$

$$i_{n_q} = i_n \sin(\beta_n) + \sum_{k=1, k \neq n}^{\infty} i_k \sin(-\Gamma_k [\Gamma_n n - \Gamma_k k](\omega_s t) + \beta_k)$$



dc component
ac component

- Harmonics compensation controller using 2DF-IMC

➤ 2DF-IMC controller

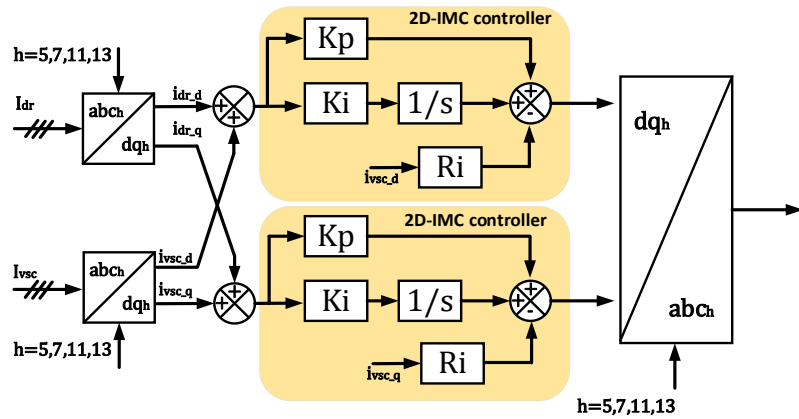

➤ PI controller

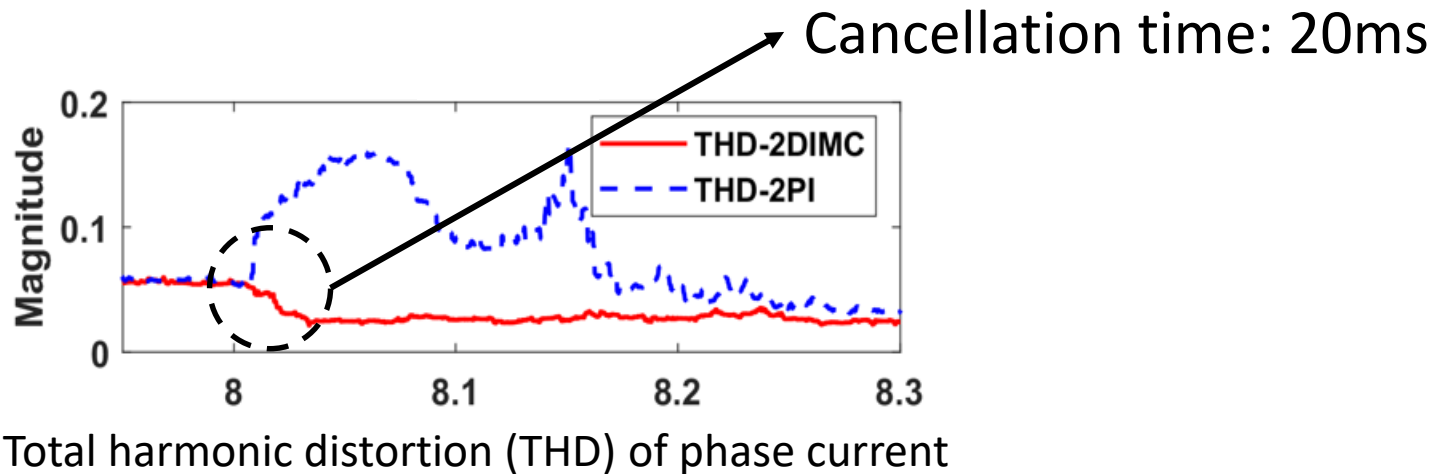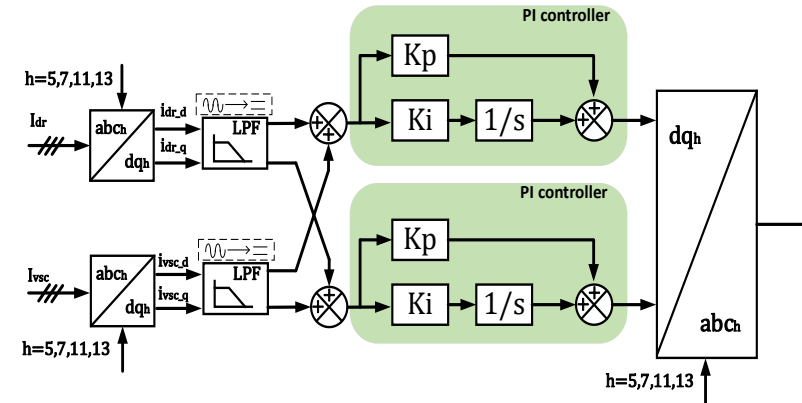

□ Conclusion and future work



Conclusion

- Hybrid converter based on 6P-DR and VSC used for offshore HVDC system
- Low cost, simple structure in offshore converter station
- Using 2DF-IMC controller replace PI controller in harmonics compensation control loop

Future work

- Exploring the size of hybrid converter components (diode rectifier, VSC converter)
- Hardware



Many thanks!



University of
Strathclyde
Glasgow